



EE1005 – Digital Logic Design Quiz# 3

Instructor: Muhammad Adeel Tahir

Section: SE-2B

Time: 20 Minutes

Name: _____

Roll No: _____



Total: 20 marks

Note: Use the back side of the page if needed. Make sure the handwriting is neat and clean while drawing the circuit, quiz will be marked as 0 if attempted in a writing that is not readable at all. **Proper labelling of each output is compulsory. Cutting will lead to negative marks.**

Q1: Simplify the following function, and implement them with two-level NAND gate circuits:

(5+5=10 marks)

$$F(A, B, C, D) = A'B'C'D + CD + AC'D$$

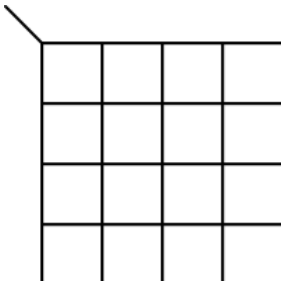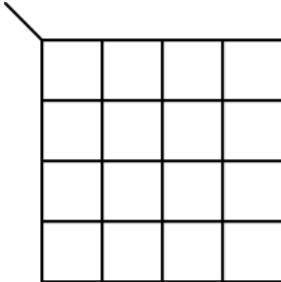


Working:

Circuit Diagram:

Q2: Simplify the Boolean function $F(w, x, y, z) = \Sigma(4, 5, 6, 7, 12)$ with don't care function

$d(w, x, y, z) = \Sigma(0, 8, 13)$. Also draw the circuit diagram.

(2 marks)

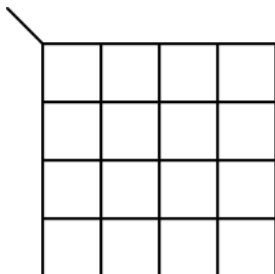

F = _____

Circuit Diagram:

Q3: Implement the following function F using 2 Input NOR gates only for 1st level and 4-Input NOR gate for 2nd level:

(4+4=8 marks)

$$F = \Sigma(0, 3, 12, 15)$$