



# National University

of Computer and Emerging Sciences Chiniot -Faisalabad Campus



## EE1005 – Digital Logic Design Quiz# 3

Instructor: Muhammad Adeel Tahir Section: SE – 2A

Time: 20 Minutes

Name: \_\_\_\_\_


Roll No: \_\_\_\_\_

Total: 20 marks

**Note:** Use the back side of the page if needed. Make sure the handwriting is neat while drawing the circuit, quiz will be marked as 0 if attempted in a writing that is not readable at all. **Cutting will result in negative marking.**

 **Q1:** Draw a NAND logic diagram that implements the complement of the following function, use 2 input NAND gate for your implementation, label each output of gate carefully to avoid deduction of marks. Use the given k-map box, avoid cutting to show proper groupings. (5+5 = 10 marks)

$$F(A, B, C, D) = \Sigma(0, 1, 2, 3, 6, 10, 11, 14)$$



$G(A, B, C, D) =$  \_\_\_\_\_

Circuit Diagram:

**Q2:** Implement and draw circuit for the following Boolean function F, together with the don't-care conditions d, using no more than two NOR gates. Use the given k-map box, avoid cutting to show proper groupings. (5+5 = 10 marks)

$$F(A, B, C, D) = \Sigma(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \Sigma(0, 1, 5, 8)$$

