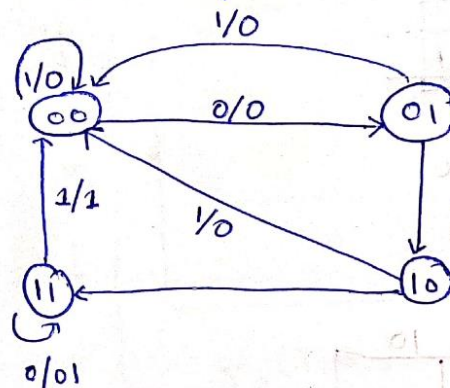


**Question Number 1****[3 + 2 + 3 + 2 = 10 Marks]**

Design a sequential circuit by using D Flip Flop to detect the sequence of three or more 0's in an input sequence of bits. The output of the circuit should be 1 when three or more 0's appears at the input, otherwise the output should be 0. You can complete your design by constructing

- State Diagram
- State Table
- Flip Flop Input Equations
- Circuit Diagram

**• State Diagram::****• State Table::**

Present state		Input		Next state		Output
A	B	x		A(t+1)	B(t+1)	y
0	0	0		0	1	0
0	0	1		0	0	0
0	1	0		1	0	0
0	1	1		0	0	0
1	0	0		1	1	0
1	0	1		0	0	0
1	1	0		1	1	1
1	1	1		0	0	1

## • Flip-Flop Input equations:-

	Bx	00	01	11	10
A	0				1
	1	1			1

$$A(t+1) = Bx' + Ax'$$

$$= x'(A+B)$$

	Bx	00	01	11	10
A	0	1			
	1	1			1


$$B(t+1) = Bx' + Ax'$$

$$= x'(A+B)$$

	Bx	00	01	11	10
A	0				
	1			1	1

$$y = AB$$

● Circuit Diagram:-

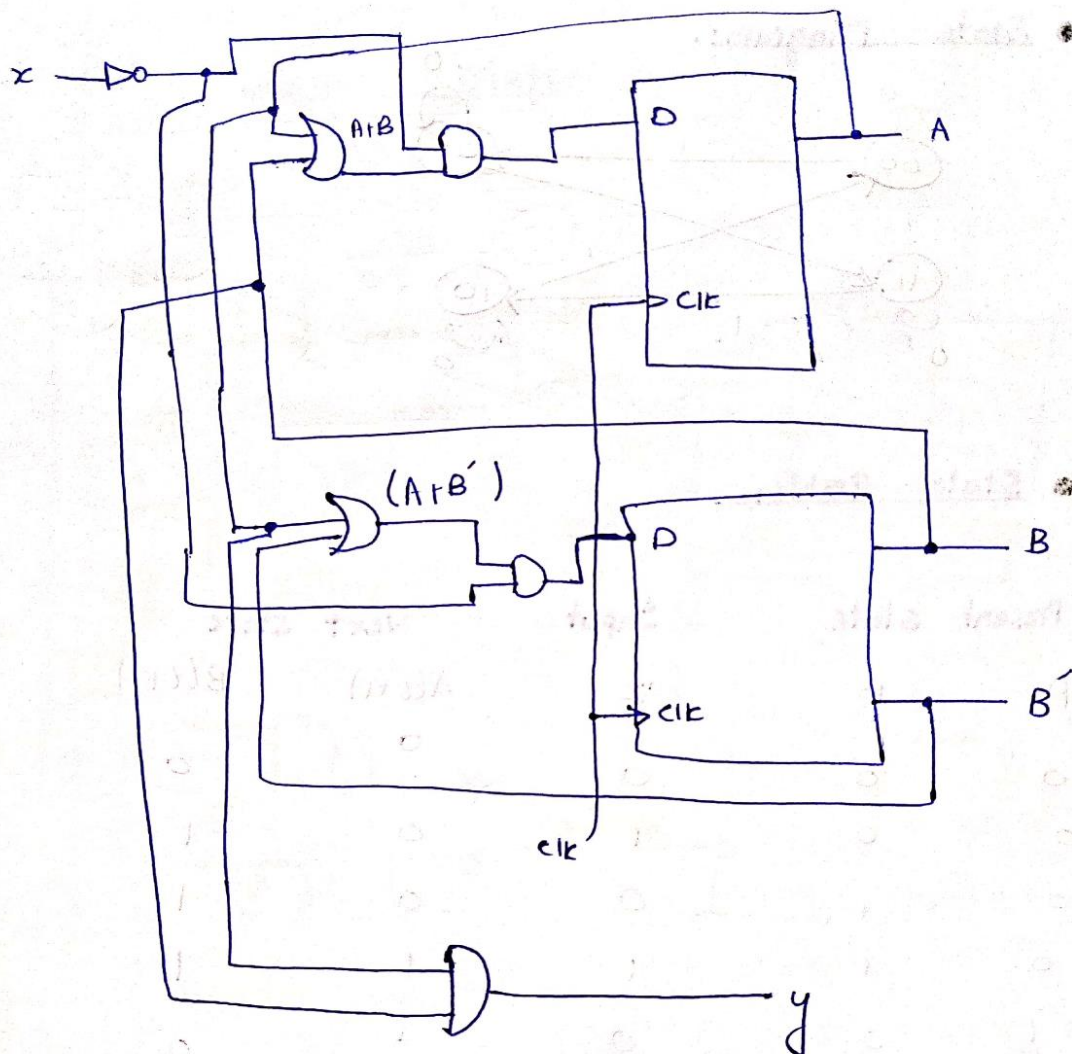


### Question Number 2

[3 + 2 + 3 + 2 = 10 Marks]

Design a sequential circuit with two D flip-flops A and B, and one input x. When x = 0, the state of the circuit remains the same. When x = 1, the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats. Complete your design by constructing

- State Diagram
- State Table
- Flip Flop Input Equations
- Circuit Diagram

Question no. 2

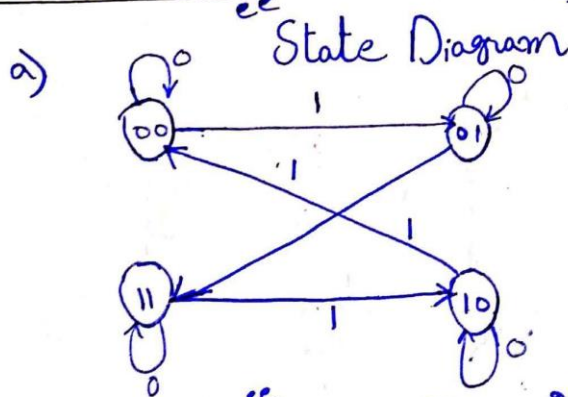

b) State Table

Present State		Input	Next State	
A	B	x	A	B
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0


c) Equations

$D_A = Ax + Bx$

$D_B = A'x + Bx'$



## “Circuit Diagram”

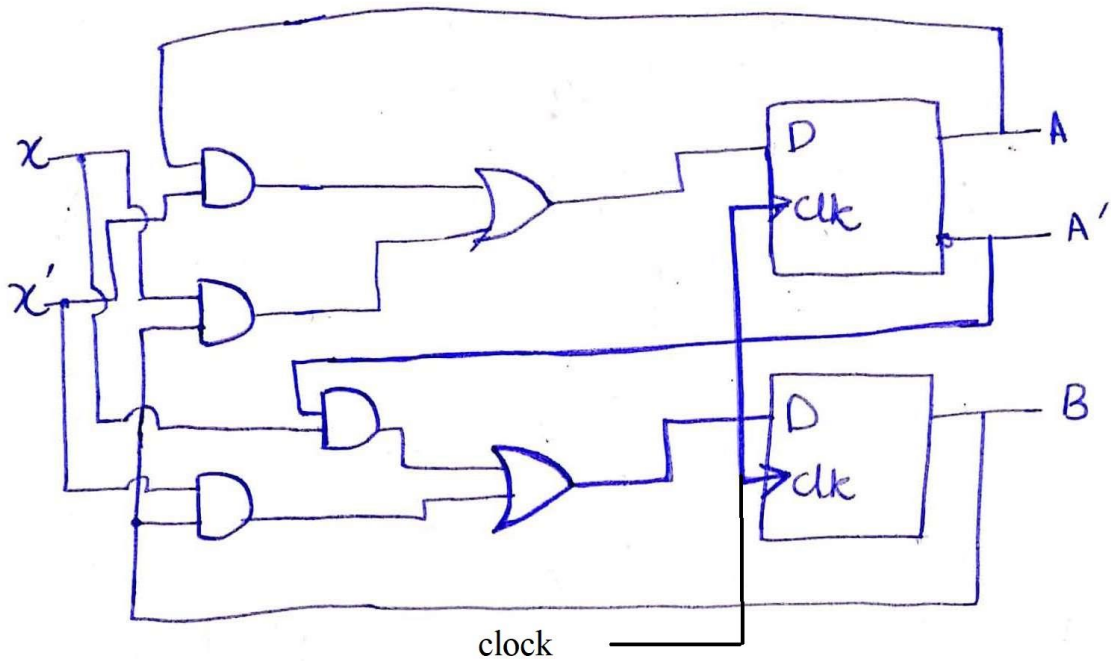

### Question Number 3


[3 + 2 + 2 + 3 + 2 = 12 Marks]

Design a sequential circuit with two JK flip-flops A and B, and one input x. When  $x = 0$ , the state of the circuit remains the same. When  $x = 1$ , the circuit goes through the state transitions from 00 to 11, to 01, to 10, back to 00, and repeats. Complete your design by finding:

- State Diagram
- State Table
- Flip Flop Inputs
- Flip Flop Input Equation
- Circuit Diagram

Question no. 3:

State Diagram

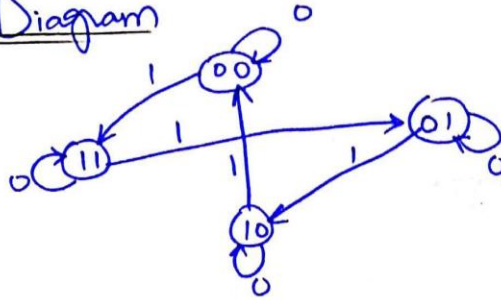

State Table and FF inputs.

Present State		Input X	Next State		FF inputs			
A	B		A	B	JA	KA	JB	KB
0	0	0	0	0	0	x	0	x
0	0	1	1	1	1	x	1	x
0	1	0	0	1	0	x	x	0
0	1	1	1	0	1	x	x	1
1	0	0	1	0	x	0	0	x
1	0	1	0	0	x	1	0	x
1	1	0	1	1	x	0	x	0
1	1	1	0	1	x	1	x	0

Flip flop input equations.

**JA**

B \ A	00	01	11	10
0	0	1	1	0
1	x	x	x	x

$$JA = x$$

**JB**

B \ A	00	01	11	10
0	0	1	x	x
1	0	0	x	x

$$JB = A'x$$

**KA**

B \ A	00	01	11	10
0	x	x	x	x
1	0	1	1	0

$$KA = x$$

**KB**


B \ A	00	01	11	10
0	x	x	1	0
1	x	x	0	0

$$KB = A'x$$

$$K_A = x$$

$$K_B = A'x$$

logic Diagram

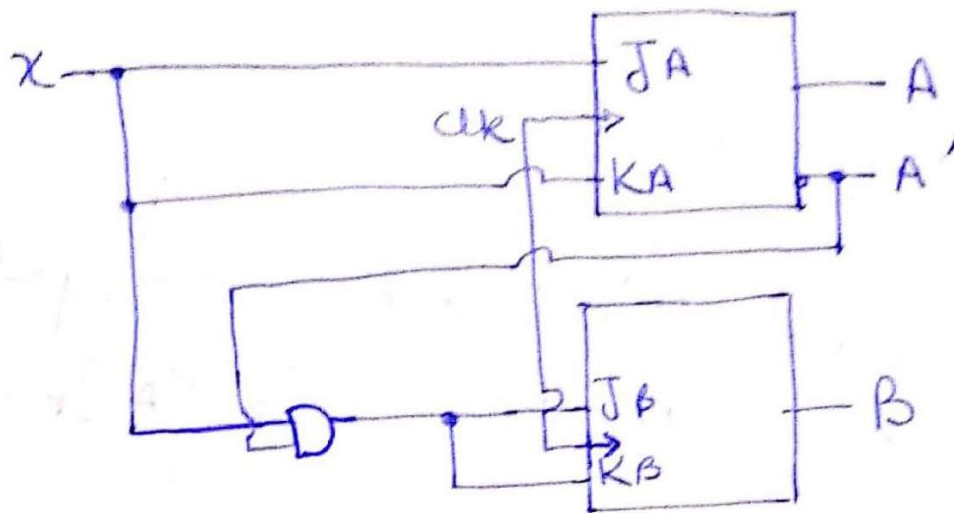


#### Question Number 4

[10 + 12 + 12 = 34 Marks]


A sequential circuit has three flip-flops A, B, C ; one input  $x$ ; and one output  $y$ . The state diagram is shown in figure below. The circuit is to be designed by treating the unused states as don't-care conditions.

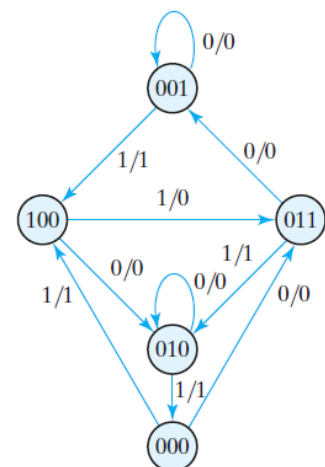- Use D Flip Flops for design
- Use JK Flip Flops for desing
- Use T Flip Flops for design



i. With D Flip Flop

Present State			Input $x$	Next State			Output $y$
A	B	C		A	B	C	
0	0	0	0	0	1	1	0
0	0	0	1	1	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	1
1	0	0	0	0	1	0	0
1	0	0	1	0	1	1	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

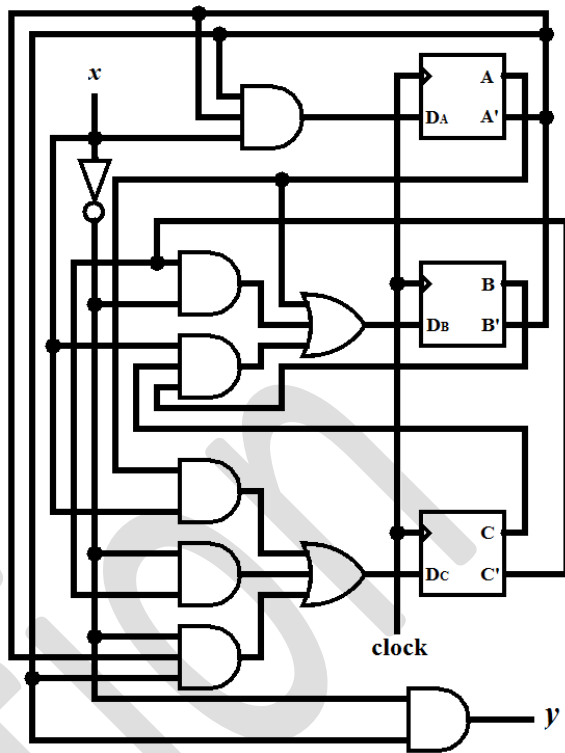

AB	Cx			
	00	01	11	10
00		1	1	
01				
11	X	X	X	X
10			X	X

$$D_A = A'B'x$$

AB	Cx			
	00	01	11	10
00	1			
01	1		1	
11	X	X	X	X
10	1	1	X	X

$$D_B = A + C'x' + BCx$$

AB	Cx			
	00	01	11	10
00	1			1
01				1
11	X	X	X	X
10		1	X	X

$$D_C = Ax + Cx' + A'B'x'$$

AB	Cx			
	00	01	11	10
00		1	1	
01		1	1	
11	X	X	X	X
10			X	X

$$y = A'x$$



ii. With JK Flip Flop

Present State			Input	Next State			Output	Flip Flop Inputs					
A	B	C	x	A	B	C	y	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	1	1	0	0	X	1	X	1	X
0	0	0	1	1	0	0	1	1	X	0	X	0	X
0	0	1	0	0	0	1	0	0	X	0	X	X	0
0	0	1	1	1	0	0	1	1	X	0	X	X	1
0	1	0	0	0	1	0	0	0	X	X	0	0	X
0	1	0	1	0	0	0	1	0	X	X	1	0	X
0	1	1	0	0	0	1	0	0	X	X	1	X	0
0	1	1	1	0	1	0	1	0	X	X	0	X	1
1	0	0	0	0	1	0	0	X	1	1	X	0	X
1	0	0	1	0	1	1	0	X	1	1	X	1	X
1	0	1	0	X	X	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X	X	X


By using k-maps the equations for J<sub>A</sub>, K<sub>A</sub>, J<sub>B</sub>, K<sub>B</sub>, J<sub>C</sub>, K<sub>C</sub> and y can be found.

$$\begin{aligned}
 J_A &= B'x & K_A &= 1 \\
 J_B &= A + C'x' & K_B &= C'x + Cx' \\
 J_C &= Ax + A'B'x' & K_C &= x \\
 y &= A'x
 \end{aligned}$$

The above equations can be used to draw the circuit diagram

iii. With T Flip Flops

Present State			Input	Next State			Output	Flip Flop Inputs		
A	B	C	x	A	B	C	y	T <sub>A</sub>	T <sub>B</sub>	T <sub>C</sub>
0	0	0	0	0	1	1	0	0	1	1
0	0	0	1	1	0	0	1	1	0	0
0	0	1	0	0	0	1	0	0	0	0
0	0	1	1	1	0	0	1	1	0	1
0	1	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	1	0	1	0
0	1	1	0	0	0	1	0	0	1	0
0	1	1	1	0	1	0	1	0	0	1
1	0	0	0	0	1	0	0	1	1	0
1	0	0	1	0	1	1	0	1	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

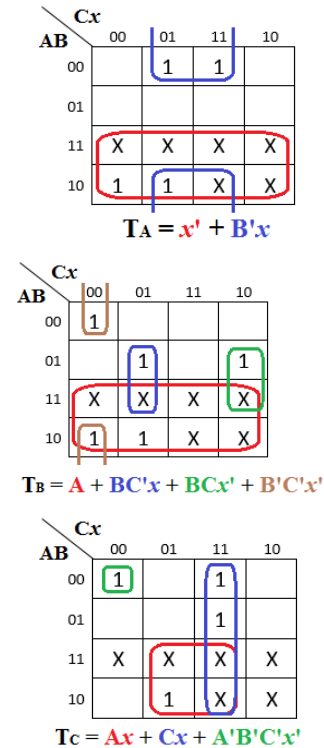

The above equations can be used to draw circuit diagram.

**Question Number 5****[3 + 8 + 3 = 14 Marks]**

For the following state table:

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>c</i>	0	0
<i>c</i>	<i>f</i>	<i>e</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>e</i>	<i>d</i>	<i>c</i>	0	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>h</i>	0	1
<i>h</i>	<i>g</i>	<i>a</i>	1	0

- Draw the corresponding state diagram.
- Tabulate the reduced state table.
- Draw the state diagram corresponding to the reduced state table

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	f	b	0	0
b	d	c	0	0
c	f	e	0	0
d	g	a	1	0
e	d	c	0	0
f	f	b	1	1
g	g	h	0	1
h	g	a	1	0

States b and e are equivalent, and d and h are also equivalent. So, removing e and h, and then replacing e and h with b and d respectively in remaining table we get.

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	f	b	0	0
b	d	c	0	0
c	f	b	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

States a and c are equivalent, removing c and replacing c with a in remaining table, we get.

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
a	f	b	0	0
b	d	a	0	0
d	g	a	1	0
f	f	b	1	1
g	g	d	0	1

There are no more equivalent states, so this is the reduced state table.

State diagrams can be drawn from the given and reduced state tables easily.