



## EE1005 – Digital Logic Design

### Assignment 3

### Spring 2024

**Instructor:** Muhammad Adeel Tahir  
**Sections:** BS-CS 2F, BS-SE 2A, BS-SE 2B

**Maximum Marks:** 100

**Due Date:** Tuesday, 19 March 2024

- Partially or fully **copied assignments** will be marked as **zero**.
- Only **handwritten** solution on **A4 page** will be accepted.
- Submission on the GCR by the deadline is **Compulsory**.
- Late submissions are not allowed. In case of late submission, assignment will not be accepted.
- Clearly indicate all the calculations in your solution. No points will be awarded in case of missing calculations.
- You can submit your assignment **during the class** on due date. But submitting on GCR as mentioned is compulsory.

#### Question Number 1

(5 + 2.5 + 2.5 = 10 marks)

Draw the two-level NAND implementation of the following Boolean functions.

- a)  $F(w, x, y, z) = \Sigma(2, 3, 4, 5, 7, 8, 10, 13, 15)$
- b)  $F(A, B, C, D) = AC'D' + A'C + ABC + AB'C + A'C'D'$
- c)  $F(A, B, C, D, E) = A.B + C.D + E$

#### Question Number 2

(5 + 5 = 10 marks)

Draw the two level NOR implementation of the following Boolean functions.

- a)  $F(w, x, y, z) = \Sigma(0, 2, 3, 8, 9, 12, 13, 15)$
- b)  $F(A, B, C, D) = \Pi(0, 2, 3, 9, 11, 12, 13, 15)$

#### Note

For NAND implementation, the first level of gates must be with AND-Invert symbols.

For NOR implementation, the first level of gates must be with OR-Invert symbols.

#### Question Number 3

(10 + 10 = 20 marks)

Draw the two-level NAND and NOR implementations of the following Boolean function F, together with the don't-care conditions d.

- a)  $F(A, B, C, D) = \Sigma(0, 6, 8, 13, 14)$        $d(A, B, C, D) = \Sigma(2, 4, 10)$
- b)  $F(A, B, C, D) = \Pi(2, 5, 6, 7, 12, 13, 14)$        $d(A, B, C, D) = \Pi(3, 9, 11, 15)$

**Question Number 4****(2+2+2+2+2=10 marks)**

The simplified Boolean functions are given below. Draw their equivalent k-maps.

- a)  $F(A,B,C) = AB + BC + A'B'C'$
- b)  $F(A,B,C) = B' + A'C' + AC$
- c)  $F(A,B,C,D) = A'B + A'C' + AB'D$
- d)  $F(A,B,C,D) = D' + AB'C + BC'$
- e)  $F(A, B, C, D) = B + A'C + AC'D$

*Note:* A neat and clean diagram is necessary for this question, properly show grouping or no marks will be given.

**Question Number 5****(10 marks)**

Implement the circuit by using 2-input NAND gates only.

$$F(A, B, C, D) = \overline{\overline{AC}} \cdot \overline{\overline{BC}} \cdot \overline{\overline{ABC}}$$

*Note:* To gain maximum marks, label each output carefully and it must be in neat handwriting. In case, the circuit labelling is not readable, partial or no marks will be given.

**Question Number 6****(4 + 6 = 10 marks)**

Simplify the following Boolean expression by using k-map and POS form and then implement the circuit by using 2-input NOR gates.

$$F(A, B, C, D) = A'B'C'D + CD + AC'D$$


**Question Number 7****(10 marks)**

Draw the multi-level NOR circuit for the following expression:

$$F = CD(B + C)A + (BC' + DE')$$

**Question Number 8****(10 + 10 = 20 marks)**

Convert the following circuit to use only AND-OR gates.

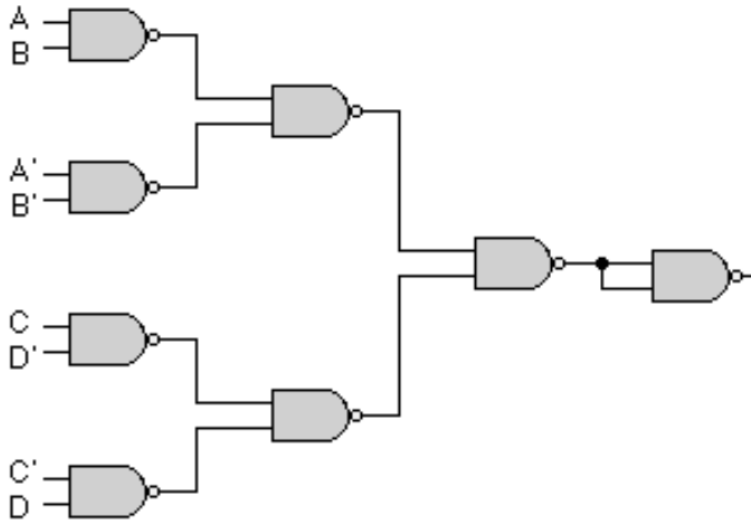**Circuit (A)****CIRCUIT (B):**