



EE1005 – Digital Logic Design Quiz# 3

Instructor: Muhammad Adeel Tahir Section: SE – 2A

Time: 20 Minutes

Name: _____

Roll No: _____

Total: 20 Marks

Note: Use the back side of the page if needed. Make sure the handwriting is neat while drawing the circuit, quiz will be marked as 0 if attempted in a writing that is not readable at all. **Cutting will result in negative marking.**

Q1: Draw a NAND logic diagram that implements the complement of the following function, use 2 input NAND gate for your implementation, label each output of gate carefully to avoid deduction of marks.

(10 marks)

$$F(A, B, C, D) = \Sigma(0,1,2,3,6,10,11,14)$$

Solution:

Marking Criteria is as followed:

- For correctly identifying the equation 5 marks are awarded.
- For correctly identifying the circuit 5 marks are awarded. Binary checking is followed in the circuit, no partial marking whatsoever.


The complement of the given function:

$$F(A, B, C, D) = \Sigma(0,1,2,3,6,10,11,14)$$

$$F' = \Sigma(4,5,7,8,9,12,13,15)$$

We plot and simplify the function G (the complement of F) using a 4-variable k-map as shown below. The simplified function is


$$G(A, B, C, D) = AC' + BC' + BD$$

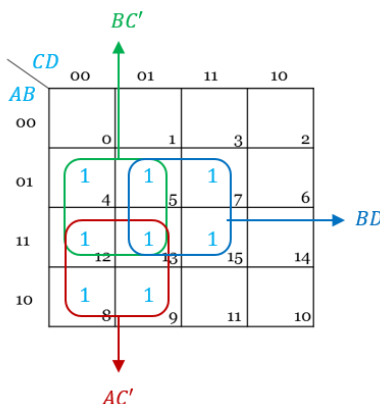

The simplified function G can be expressed as

$$G(A, B, C, D) = [G'(A, B, C, D)]' = [(AC' + BC' + BD)']' = [(AC')'(BC')'(BD)']' \Rightarrow \text{Demorgan's Theorem}$$

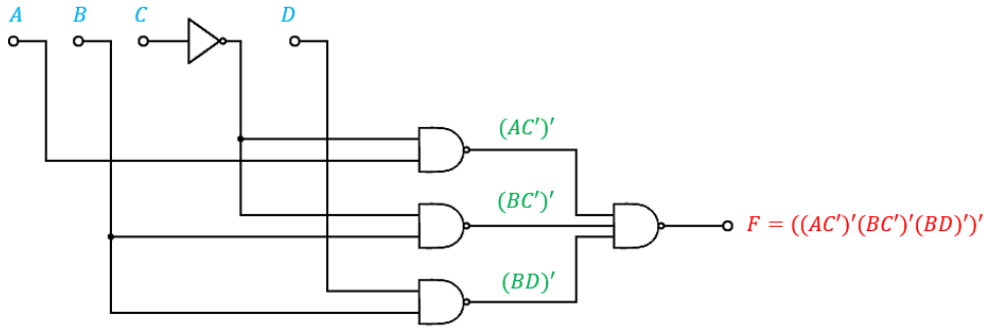Therefore, we implement this function using a two-level NAND gate circuit as shown below.



Q2: Implement the following Boolean function F, together with the don't-care conditions d , using no more than two NOR gates: (10 marks)

$$F(A, B, C, D) = \Sigma(2, 4, 10, 12, 14)$$

$$d(A, B, C, D) = \Sigma(0, 1, 5, 8)$$

Solution:

Marking Criteria is as followed:

- For correctly identifying the equation 5 marks are awarded. In case k-map is wrong, 0 is awarded.
- For correctly identifying (with steps) the circuit 5 marks are awarded. Binary checking is followed in the circuit, no partial marking whatsoever.

First, the 1's and X's of the given function:

From the 0's and X's, we obtain the simplified-complemented function:

$$F' = D + A'BC$$

Thus, the minimum product of sums for F is

$$F = D'(A + B' + C')$$

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	<i>X</i>	<i>X</i>	0	1
	01	1	<i>X</i>	0	0
	11	1	0	0	1
	10	<i>X</i>	0	0	1

A blue box highlights the cells (01, 01), (01, 11), (11, 01), and (11, 11), which correspond to the minterms $A'B'C$ and $A'BC$. A blue arrow points from this box to the label $A'BC$.
 A green box highlights the cells (01, 00), (11, 00), (01, 10), and (11, 10), which correspond to the minterms $A'B'C'$ and $A'BC'$. A green arrow points from this box to the label D .

We reformulate the function F so that it can be implemented using NOR gates as follows:

$$F = (F')' = \{ [D'(A + B' + C')]'\}' = \{ (D')' + (A + B' + C')'\}' = \{ D + (A + B' + C')'\}'$$

