

# EE1005 – Digital Logic Design

## Assignment 5 (Solution)

Spring 2023

**Maximum Marks: 70**

**Due Date:** 02 May 2023


**Instructions:**

- Partially or fully **copied assignments** will be marked as **zero**.
- Only **handwritten** solution on **A4 page** will be accepted.
- Late submissions are not allowed.
- Clearly indicate all the calculations in your solution. No points will be awarded in case of missing calculations.

### Question Number 1

 **[10 Marks]**

Construct a SR latch by using NOR gates. The latch must have an enable input. Also compute the state table of the latch stating all possible combinations of enable input and S, R inputs.




En	S	R	Q	State
1	X	X	Q	No Change
0	0	0	?	Forbidden
0	0	1	1	Set
0	1	0	0	Reset
0	1	1	?	Forbidden

 **Question Number 2****[2.5 x 4 = 10 Marks]**

Write the output Y and Q for the following four cases with proper calculations/reasons. The latches are constructed with NAND gates.

- When clock = 0
- When clock is changing from 0 to 1
- When clock = 1
- When clock is changing from 1 to 0




- 1) When clock = 0
  - Master latch is enable
  - Slave latch is disable
  - $Y = D$
  - Q is unchanged
- 2) When clock is changing from 0 to 1
  - Master latch is disabled
  - Slave latch is enable
  - $Q = Y$  (the value of D will appear at Q at positive edge of clock)
- 3) When clock = 1
  - Master latch is disabled
  - Slave latch is enable
  - Change in D will not affect Q
- 4) When clock is changing from 1 to 0
  - Master latch is enable
  - Slave latch is disable
  - Change in D will not affect Q

**It is a positive edge trigger D flip flop**

**Question Number 3****[2.5 x 4 = 10 Marks]**

Write the output of each gate for the following four cases with proper reasons/calculations.

- When clock = 0
- When clock is changing from 0 to 1
- When clock = 1
- When clock is changing from 1 to 0

 **1) When clock = 0**

- $G2 = (0.G1)' = 1$
- $G3 = (0.G2.G4)' = 1$
- $S = R = 1$
- $D = X$
- No change in state

**2) When clock is changing from 0 to 1**

- $D = 0$
- $G1 = (1.0)' = 1$
- $S = G2 = (1.1)' = 0$
- $R = G3 = (1.0.G4)' = 1$
- $G4 = (1.1)' = 0$
- $Q = 1$  (Set State)

**3) When clock is changing from 0 to 1**

- $D = 1$
- $G1 = (1.1)' = 0$
- $S = G2 = (1.0)' = 1$
- $G4 = (0.1)' = 1$
- $R = G3 = (1.1.1)' = 0$
- $Q = 0$  (Reset State)

**4) When clock = 1**

- No further change in state as discussed in above two cases

**5) When clock is changing from 1 to 0**


- $G2 = (0.G1)' = 1$
- $G3 = (0.G2.G4)' = 1$
- $S = R = 1$
- $D = X$
- No change in state

**It is a positive edge trigger D flip flop**

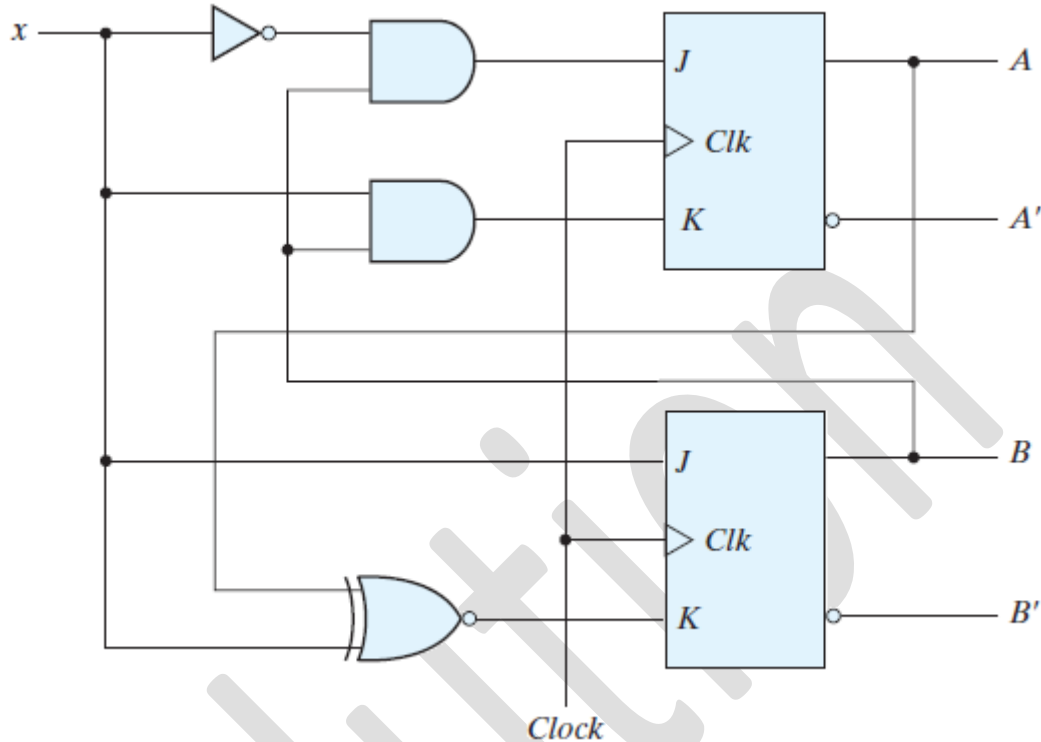**Question Number 4****[4 + 4 + 2 = 10 Marks]**

Analyze the following combinational circuit to find its

- State equation(s)
- State table
- State diagram



From circuit diagram

$$J_A = x'B \quad K_A = xB$$

$$J_B = x \quad K_B = (x \oplus A)'$$

For JK Flop flop we have


$$Q(t+1) = JQ' + K'Q$$

For Flip Flop A

$$A = x'BA' + (xB)'A$$

For Flip Flop B

$$B = xB' + (x \oplus A)B$$

 


Present State		Input					Next State	
A	B	x	$x'BA'$	$(xB)'A$	$xB'$	$(x \oplus A)B$	A	B
0	0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0	1
0	1	0	1	0	0	0	1	0
0	1	1	0	0	0	1	0	1
1	0	0	0	1	0	0	1	0
1	0	1	0	1	1	0	1	1
1	1	0	0	1	0	1	1	1
1	1	1	0	0	0	0	0	0

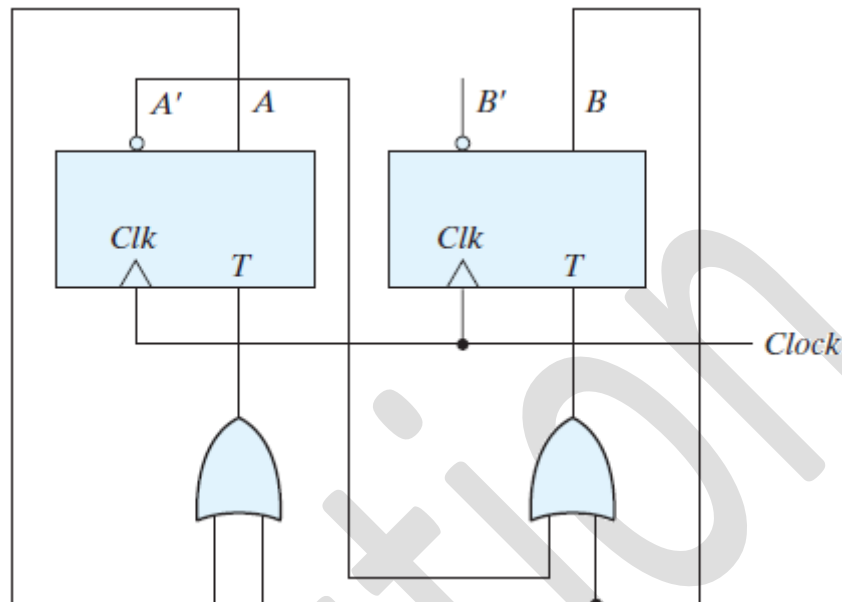**Question Number 5****[4 + 4 + 2 = 10 Marks]**

Analyze the following combinational circuit to find its

- State equation(s)
- State table
- State diagram



From circuit diagram

$$T_A = AB$$

$$T_B = A'B$$

For T Flop flop we have


$$Q(t + 1) = T \oplus Q$$

For Flip Flop A

$$A = AB \oplus A$$

For Flip Flop B

$$B = A'B \oplus B$$

 

Present State				Next State	
A	B	A'B	AB	A	B
0	0	0	0	0	0
0	1	1	0	0	0
1	0	0	0	1	0
1	1	0	1	0	1

**Question Number 6****[4 + 4 + 2 = 10 Marks]**


A sequential circuit with two D flip-flops A and B, two inputs, x and y ; and one output z is specified by the following next-state and output equations.

$$A(t + 1) = xy' + xB$$

$$B(t + 1) = xA + xB'$$

$$z = A$$

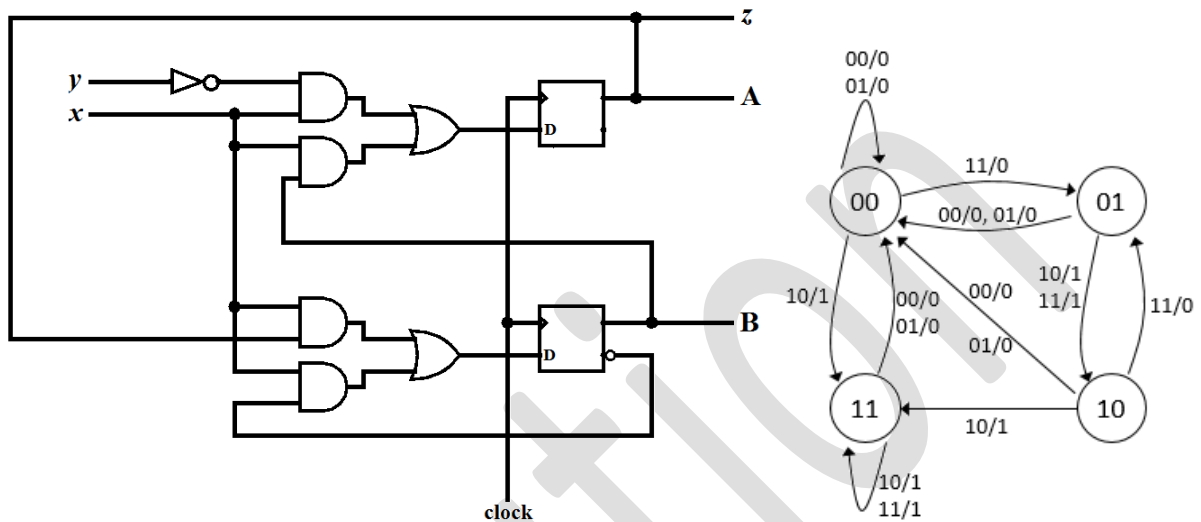- Draw the logic diagram of the circuit
- List the state table for the sequential circuit
- Draw the corresponding state diagram




Present State		Inputs						Next State		Output
A	B	x	y	$xy'$	$xB$	$xA$	$xB'$	A	B	z
0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	1	1	1
0	0	1	1	0	0	0	1	0	1	0
0	1	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0
0	1	1	0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0	1	0	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0
1	0	1	0	1	0	1	1	1	1	1
1	0	1	1	0	0	1	1	0	1	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	1	1	1	0	1	1	1
1	1	1	1	0	1	1	0	1	1	1

**Question Number 7****[5 + 5 = 10 Marks]**

A sequential circuit has one flip-flop Q, two inputs x and y, and one output S. It consists of a full-adder circuit connected to a D flip-flop, as shown in figure below.

Derive the:

 - State table and
- State diagram of the sequential circuit.



Present State	Inputs		Output		Next State
Q	x	y	S	C	Q
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1

