

**5.17** Design a one-input, one-output serial 2's complementer. The circuit accepts a string of bits from the input and generates the 2's complement at the output. The circuit can be reset asynchronously to start and end the operation. (HDL—see Problem 5.39)

*(The circuit is identical to the JK flip-flop A and B and two inputs  $E$  and  $F$ . If*

Solution → Suppose we have —


01001110101100

2's complement → 10110001010100

State table

Present state A	Input x	Next state A(t+1)	Output y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

State Diagram

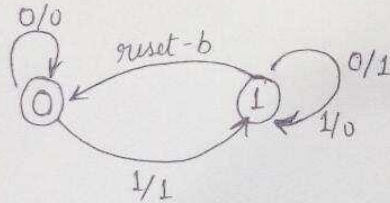

K-map for A(t+1)

$$A(t+1) = A + x$$

$$D_A = A + x$$

A \ x	0	1
0	0	1
1	1	1


K-map for y

$$y = Ax' + A'x$$

$$y = A \oplus x$$

A \ x	0	1
0	0	1
1	1	0

Design

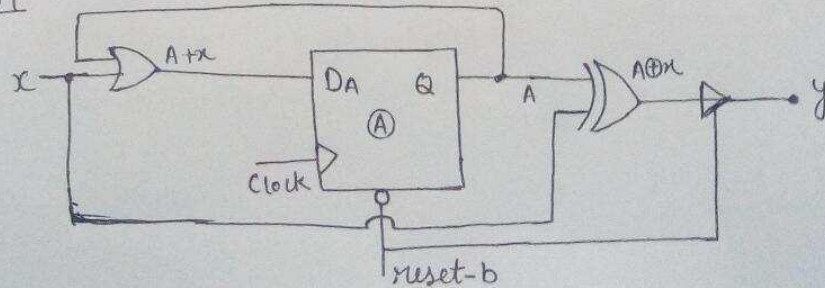


<https://www.youtube.com/watch?v=aHgM51UaFmc>

### Question 2:

Where  $z = \text{cin}$  and  $x, y = A$  and  $B$  (inputs at select lines as shown in diagram)

$x$	$y$	$z$	$S$	$C$	
0	0	0	0	0	} $S = z, C = 0$
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	} $S = z', C = z$
1	0	0	1	0	
1	0	1	0	1	} $S = z', C = z$
1	1	0	0	1	
1	1	1	1	1	} $S = z, C = 1$

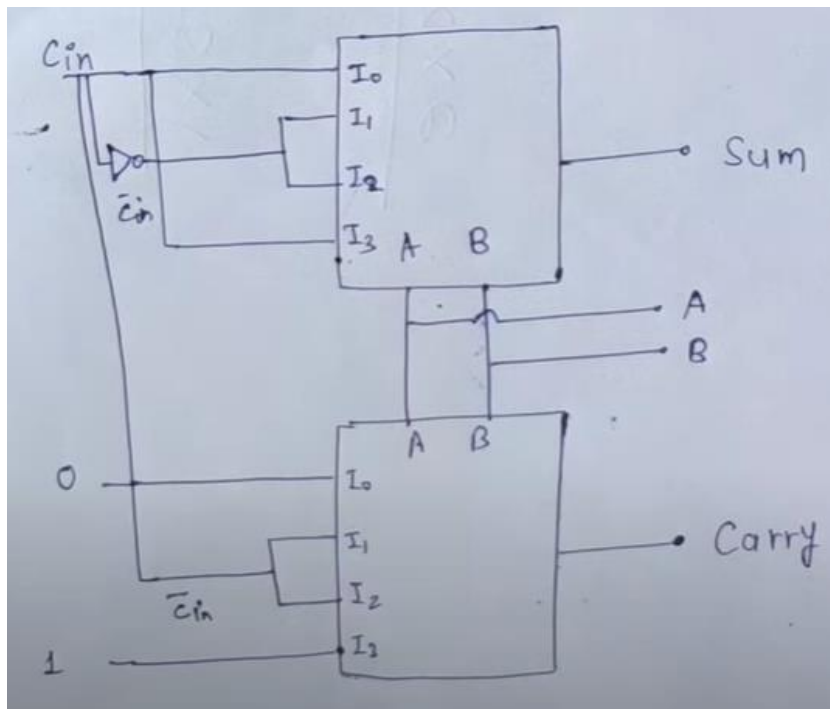

### Question 3:

From the figure we can write that:

$$J_A = A + B$$

$$K_A = x + A' + B'$$

$$T_B = A$$

$$y = (x + B + B')'$$

#### State Equations

$$A(t+1) = J_A A' + K_A A = (A + B)A' + (x + A' + B')A = A'B + x'AB$$


$$B(t+1) = T_B \oplus B = A \oplus B$$

$$y = (x + B + B')' = (x + 1)' = 0$$

State Table

Present State		Input		Next State		Output	
A	B	x	A'B	x'AB	A(t+1)	B(t+1)	y
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	1	0	1	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	0	1	0
1	0	1	0	0	0	1	0
1	1	0	0	1	1	0	0
1	1	1	0	0	0	0	0

State Diagram

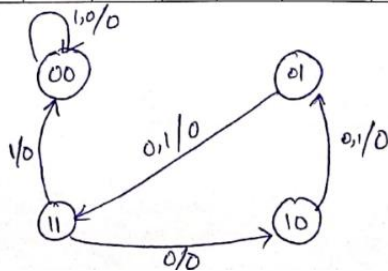

#### Question 4:

##### Part (i)

F and H are equivalent, remove H and replace H with F.  
After replacing H with F

E and G are equivalent, remove G and replace G with E.  
C and D are equivalent, remove D and replace D with C.

After making the above replacements

B and E are equivalent, remove E and replace E with B.

The reduced state table is

Present State	Next State		Output	
	x = 0	x = 1	x = 0	x = 1
A	A	B	1	0
B	C	F	0	1
C	B	F	1	0
F	F	B	1	1


##### Part (ii)

As there are 8 states in the given table. So, we need 3 flip flops to design the circuit.


##### Part (iii)

In the reduced state table there are 4 states, hence we need 2 flip flops to design the circuit given by reduced state table.

##### Part (iv)

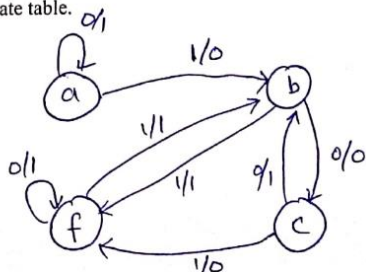


### Question 5:

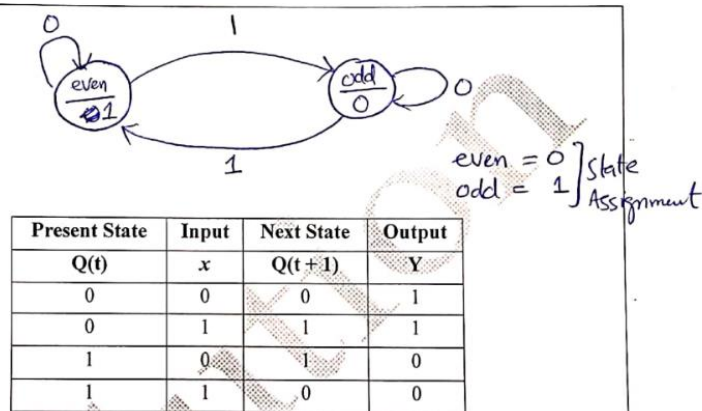

For a D flip flop  $Q(t+1) = D$ , hence we need to find the equations of D and Y. From the table it can be clearly seen that:

$$D = Q \oplus X$$

$$Y = Q'$$

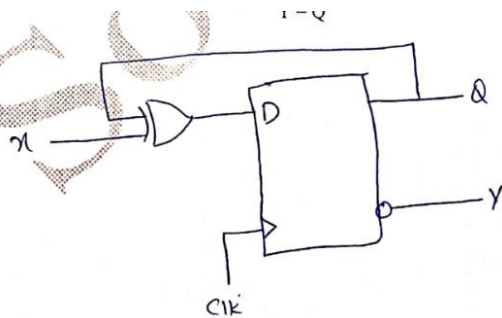

### Question 6:

#### Question 1: Multiplexer (MUX)

**What is the function of a 4-to-1 multiplexer?** A) Combines four inputs into one output. B) Selects one of four inputs to output. C) Divides one input into four outputs. D) Encodes four inputs into fewer lines.

**Answer: B)** Selects one of four inputs to output.

#### Question 2: Decoders

**What is true about a 2-to-4 line decoder?** A) Activates multiple outputs at a time. B) Has 4 inputs and 2 outputs. C) Has 2 inputs and 4 outputs, one active at a time. D) All outputs are always active.

**Answer: C)** Has 2 inputs and 4 outputs, one active at a time.

#### Question 3: Latches

**What does a D latch do?** A) Divides the clock frequency. B) Stores a bit when enabled. C) Converts serial to parallel data. D) Toggles between states.

**Answer: B)** Stores a bit when enabled.

#### Question 4: Sequential Circuits

**What feature do sequential circuits have?** A) Only arithmetic operations. B) Memory elements. C) No clock signals. D) Faster than combinational circuits.

**Answer: B)** Memory elements.

#### Question 5: Decoders and MUX

**How can decoders and multiplexers be used together?** A) Decoder enables multiplexer signals. B) Multiplexer selects decoders. C) Decoder outputs connect to multiplexer inputs. D) Multiplexer generates decoder selection lines.

**Answer: A)** Decoder enables multiplexer signals.

#### BONUS:

The answer to this riddle lies in the way the apples are taken from the basket. Here's how it could work:

1. You take an apple, leaving **four** in the basket.
2. Your friend takes an apple, leaving **three** in the basket.
3. Their friend takes the last apple, but they take it **along with the basket**.

So, the friend took both an apple and the basket, which still had one apple in it. Therefore, one apple remains in the basket. It's a clever play on words!