



EE1005 – Digital Logic Design
Quiz# 4

Instructor: Muhammad Adeel Tahir

Section: SE-2B

Time: 20 Minutes

Name: _____

Roll No: _____

Total: 15 marks

Note: Use the back side of the page if needed. Make sure the handwriting is neat and clean, quiz will be marked as 0 if attempted in a writing that is not readable at all.

Q: An **M-bit** thermometer code for the number **k** consists of **(k) 1's** in the least significant bit positions and **(M – k) 0's** in more significant bit positions. A binary-to-thermometer code converter has **N inputs** and **$2^N - 1$ outputs**. It produces a $2^N - 1$ bit thermometer code for the number specified by the input. Design a combinational circuit for binary-to-thermometer code converter provided the number of inputs = 3 by finding the following. **Also draw circuit diagram. (5 marks)** Note: Incase the truth table/equations are not correct, the question will receive 0 mark

No of Inputs: _____ **No of Outputs:** _____

(1 marks)

Truth Table:

(5 marks)

Use $A_0, A_1, A_3..$ for the inputs, and $T_0, T_1...T_n$ for the outputs

Equations:

(1.75 each = 4 marks)

--