

# EE1005 – Digital Logic Design

## Assignment 4 (Solution)

Spring 2023

Maximum Marks: 100

Due Date: 31 March 2023

### Instructions:


- Partially or fully **copied assignments** will be marked as **zero**.
- Only **handwritten** solution on **A4 page** will be accepted.
- Late submissions are not allowed.
- Clearly indicate all the calculations in your solution. No points will be awarded in case of missing calculations.
- You can submit your assignment **before 5:00 PM** on/before due date.

### Question Number 1

[5 + 4 + 1 = 10 Marks]

Analyze the following combinational circuit to find its

- Boolean function
- Truth Table

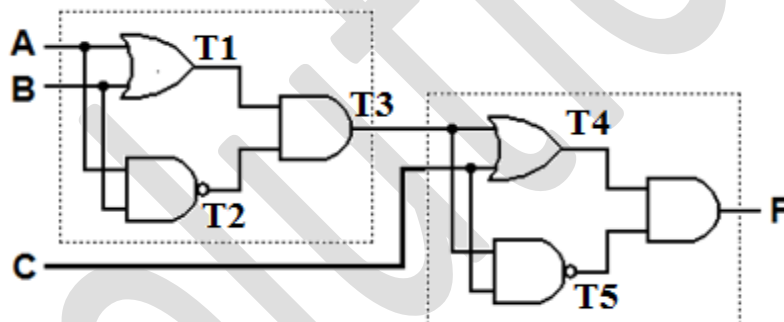

And then conclude that functionality of this circuit.

$$\begin{aligned} T1 &= A + B & T2 &= (AB)' & T3 &= T1T2 \\ T4 &= T3 + C & T5 &= (T3C)' & F &= T4T5 \end{aligned}$$

$$F = T4T5 = [(T3 + C)(T3C)'] = [(T3' + C')(T3 + C)] = T3'C + T3C'$$

$$F = (T1T2)'C + T1T2C' = (T1' + T2')C + (AB)'(A + B)C'$$

$$F = [(A + B)' + \{(AB)'\}]C + (A' + B')(A + B)C'$$

$$F = A'B'C + ABC + A'BC' + AB'C'$$

$$F = A \oplus B \oplus C$$


A	B	C	T1	T2	T3	T4	T5	F
0	0	0	0	1	0	0	1	0
0	0	1	0	1	0	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	1	0	0
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	0	0
1	1	0	1	0	0	0	1	0
1	1	1	1	0	0	1	1	1

This is a circuit of 3 input XOR function.

**Question Number 2****[5 + 4 + 1 = 10 Marks]**

Analyze the following combinational circuit to find its

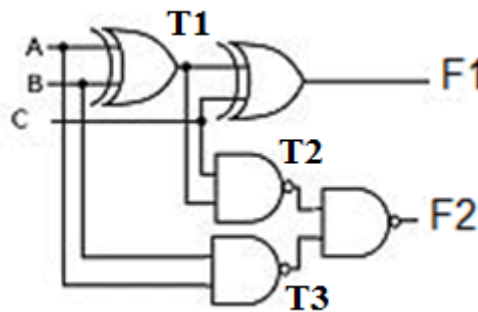- i) Boolean functions of outputs
- ii) Truth Table



And then conclude that functionality of this circuit.

$$T1 = A \oplus B \quad F1 = T1 \oplus C$$

$$T2 = (T1C)' \quad T3 = (AB)'$$

$$F2 = (T2T3)'$$

$$F1 = T1 \oplus C = A \oplus B \oplus C$$

$$F2 = (T2T3)' = T2' + T3' = ((T1C)')' + ((AB)')' = T1C + AB = (A \oplus B)C + AB$$

$$F2 = A'BC + AB'C + AB$$


A	B	C	T1	T2	T3	F1	F2
0	0	0	0	1	1	0	0
0	0	1	0	1	1	1	0
0	1	0	1	1	1	1	0
0	1	1	1	0	1	0	1
1	0	0	1	1	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	1	0	0	1
1	1	1	0	1	0	1	1

This is a circuit of a full adder. Where F1 is sum and F2 is carry.

**Question Number 3****[7 + 3 = 10 Marks]**

Analyze the following combinational circuit to find its

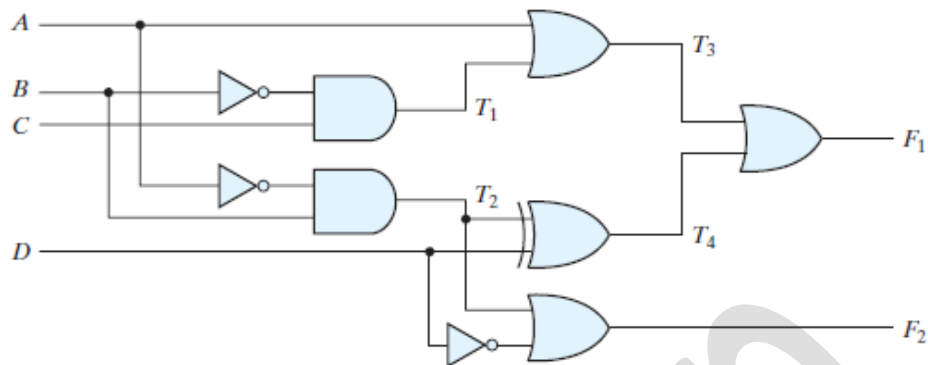- i) Boolean functions of outputs
- ii) Truth Table



$$T1 = B'C \quad T2 = A'B \quad T3 = A + T1 \quad T4 = T2 \oplus D$$

$$F1 = T3 + T4 \quad F2 = T2 + D'$$

$$F1 = T3 + T4 = A + T1 + T2 \oplus D = A + B'C + T2'D + T2D' = A + B'C + (A'B)'D + A'BD'$$

$$F1 = A + B'C + AD + B'D + A'BD'$$


$$F2 = T2 + D' = A'B + D'$$

A	B	C	D	A'	B'	D'	T1	T2	T3	T4	F1	F2
0	0	0	0	1	1	1	0	0	0	0	0	1
0	0	0	1	1	1	0	0	0	0	1	1	0
0	0	1	0	1	1	1	1	0	1	0	1	1
0	0	1	1	1	1	0	1	0	1	1	1	0
0	1	0	0	1	0	1	0	1	0	1	1	1
0	1	0	1	1	0	0	0	1	0	0	0	1
0	1	1	0	1	0	1	0	1	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	0	1
1	0	0	0	0	1	1	0	0	1	0	1	1
1	0	0	1	0	1	0	0	0	1	1	1	0
1	0	1	0	0	1	1	1	0	1	0	1	1
1	0	1	1	0	1	0	1	0	1	1	1	0
1	1	0	0	0	0	1	0	0	1	0	1	1
1	1	0	1	0	0	0	0	0	1	1	1	0
1	1	1	0	0	0	1	0	0	1	0	1	1
1	1	1	1	0	0	0	0	0	1	1	1	0

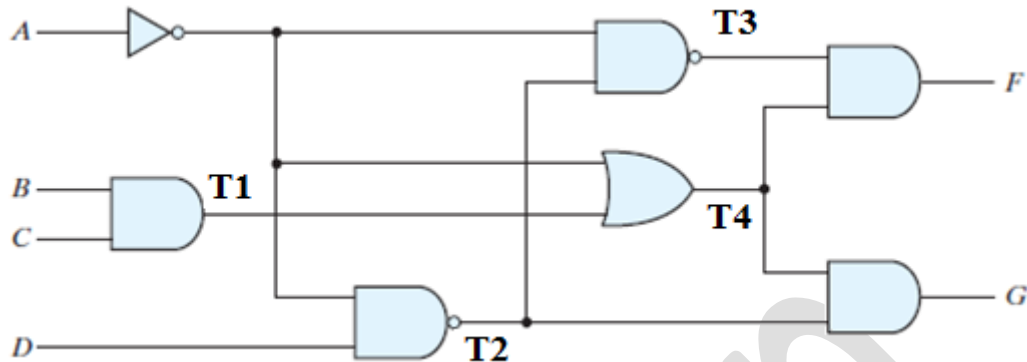**Question Number 4****[7 + 3 = 10 Marks]**

Analyze the following combinational circuit to find its

- Boolean functions of outputs
- Truth Table



$$T1 = BC \quad T2 = (A'D)'$$

$$T3 = (A'T2)'$$

$$T4 = A' + T1$$

$$F = T3T4 \quad G = T4T2$$

$$F = T3T4 = (A'T2)'(A' + T1) = (A + T2)(A' + T1) = (A + (A'D)')(A' + BC)$$

$$F = (A + A + D')(A' + BC) = (A + D')(A' + BC)$$

$$F = ABC + A'D' + BCD'$$

$$G = T4T2 = (A' + T1)(A'D)' = (A' + BC)(A + D')$$

$$G = A'D' + ABC + BCD'$$

A	B	C	D	A'	T1	T2	T3	T4	F	G
0	0	0	0	1	0	1	0	1	0	1
0	0	0	1	1	0	0	1	1	1	0
0	0	1	0	1	0	1	0	1	0	1
0	0	1	1	1	0	0	1	1	1	0
0	1	0	0	1	0	1	0	1	0	1
0	1	0	1	1	0	0	1	1	1	0
0	1	1	0	1	1	1	0	1	0	1
0	1	1	1	1	1	0	1	1	1	0
1	0	0	0	0	0	1	1	0	0	0
1	0	0	1	0	0	1	1	0	0	0
1	0	1	0	0	0	1	1	0	0	0
1	0	1	1	0	0	1	1	0	0	0
1	1	0	0	0	0	1	1	0	0	0
1	1	0	1	0	0	1	1	0	0	0
1	1	1	0	0	1	1	1	1	1	1
1	1	1	1	0	1	1	1	1	1	1


**Question Number 5****[2 + 5 + 2 + 1 = 10 Marks]**

A majority circuit is a combinational circuit whose output is equal to 1 if the input variables have more 1's than 0's. The output is 0 otherwise. Design a 4 input majority circuit by finding:


- No. of inputs and outputs
- Truth Table
- Simplified expressions of outputs
- Logic Diagram

**4 Inputs and 1 output**

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

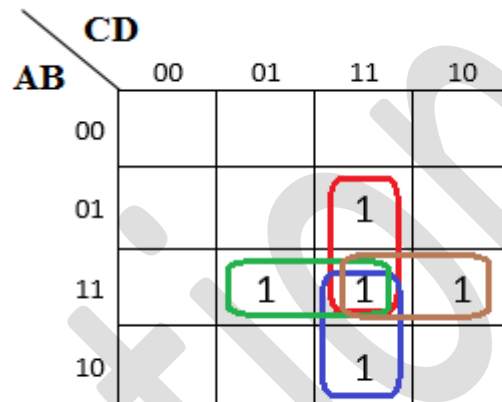

$$F = BCD + ACD + ABD + ABC$$

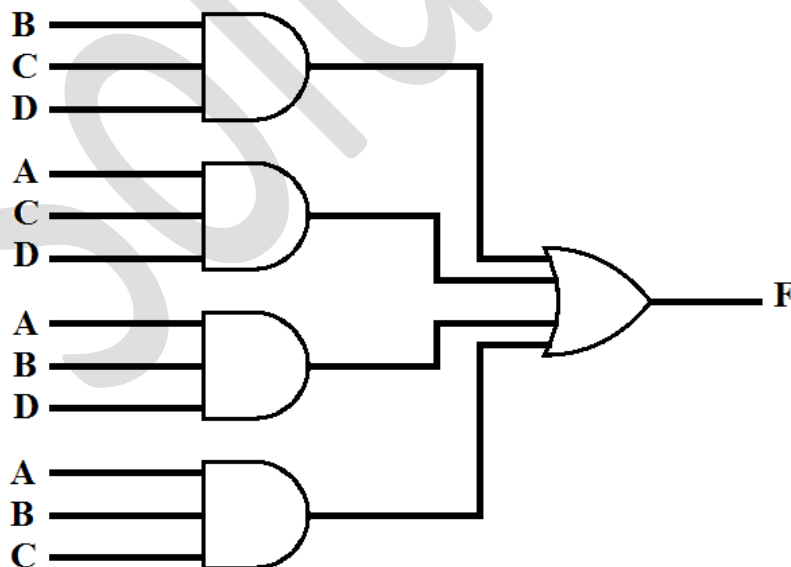

**Question Number 6****[2 + 5 + 2 + 1 = 10 Marks]**

Design a combinational circuit to convert a 4 bit gray code to 4 bit binary number. Complete your design by finding the:

- No. of input(s) and output(s)
- Truth Table
- Simplified expression(s) of output(s)
- Logic Diagram

**4 Inputs and 4 output**

G <sub>3</sub>	G <sub>2</sub>	G <sub>1</sub>	G <sub>0</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

G <sub>3</sub> G <sub>2</sub>	G <sub>1</sub> G <sub>0</sub>			
	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$$B_3 = G_3$$

G <sub>3</sub> G <sub>2</sub>	G <sub>1</sub> G <sub>0</sub>			
	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

$$B_2 = G_3'G_2 + G_3G_2'$$


$$B_2 = G_3 \oplus G_2$$

G <sub>3</sub> G <sub>2</sub>	G <sub>1</sub> G <sub>0</sub>			
	00	01	11	10
00			1	1
01	1	1		
11			1	1
10	1	1		

$$B_1 = G_3 \oplus G_2 \oplus G_1$$

G <sub>3</sub> G <sub>2</sub>	G <sub>1</sub> G <sub>0</sub>			
	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	
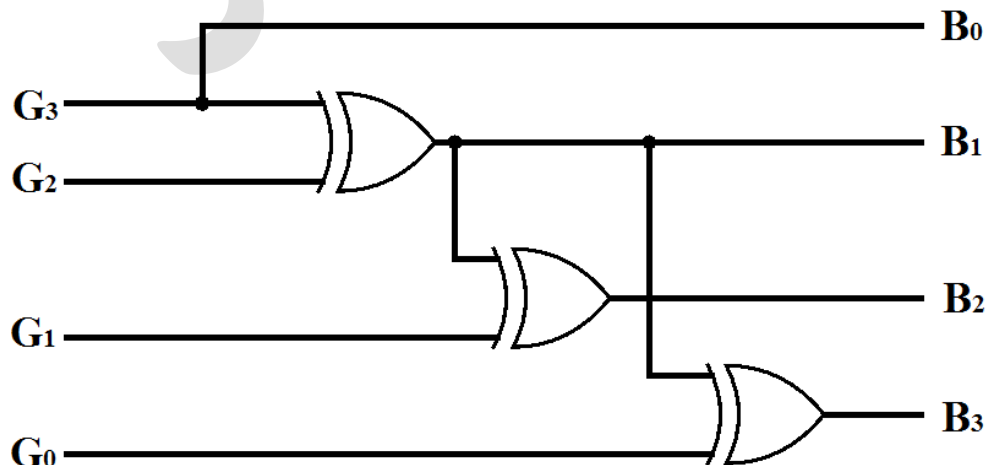
$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$



**Question Number 7****[2 + 5 + 2 + 1 = 10 Marks]**

Design a 4 bit 2's complement calculator. The output of the circuit is the 2's complement of the input binary number. Complete your design by finding the:

- No. of input(s) and output(s)
- Truth Table
- Simplified expression(s) of output(s)
- Logic Diagram

**4 Inputs and 4 output**

A	B	C	D	w	x	y	z
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	1	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	0	1
1	0	0	0	1	0	0	0
1	0	0	1	0	1	1	1
1	0	1	0	0	1	1	0
1	0	1	1	0	1	0	1
1	1	0	0	0	1	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

CD \ AB	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

$$y = C'D + CD'$$


CD \ AB	00	01	11	10
00		1	1	
01		1	1	
11		1	1	
10		1	1	

$$z = D$$

CD \ AB	00	01	11	10
00		1	1	1
01	1	1	1	1
11				
10	1			

$$w = A'C + A'D + A'BC' + AB'C'D$$

CD \ AB	00	01	11	10
00		1	1	1
01	1			
11	1			
10		1	1	1
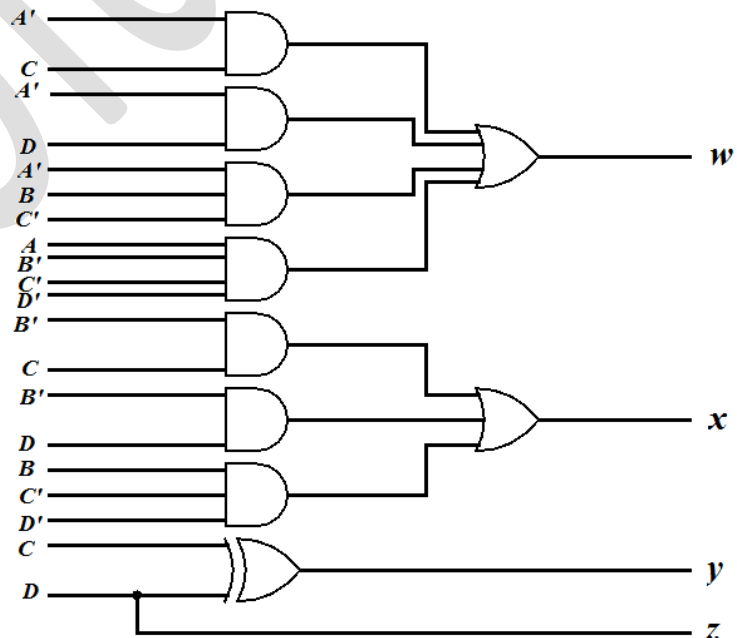
$$x = B'C + B'D + BC'D'$$


**Question Number 8****[2 + 5 + 2 + 1 = 10 Marks]**

Design a combinational circuit whose output is equal to 1 when input is an odd number and multiple of 3, otherwise the output is 0. Your circuit should be capable of taking the input from 0 to 15. Complete your design by finding the:

- No. of input(s) and output(s)
- Truth Table
- Simplified expression(s) of output(s)
- Logic Diagram

**4 Inputs and 1 output**


A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

CD \ AB	00	01	11	10
00			1	
01				
11			1	
10		1		

$$F = A'B'CD + ABCD + AB'C'D$$

$$F = CD(A'B' + AB) + AB'C'D$$

$$F = CD(A \oplus B)' + AB'C'D$$

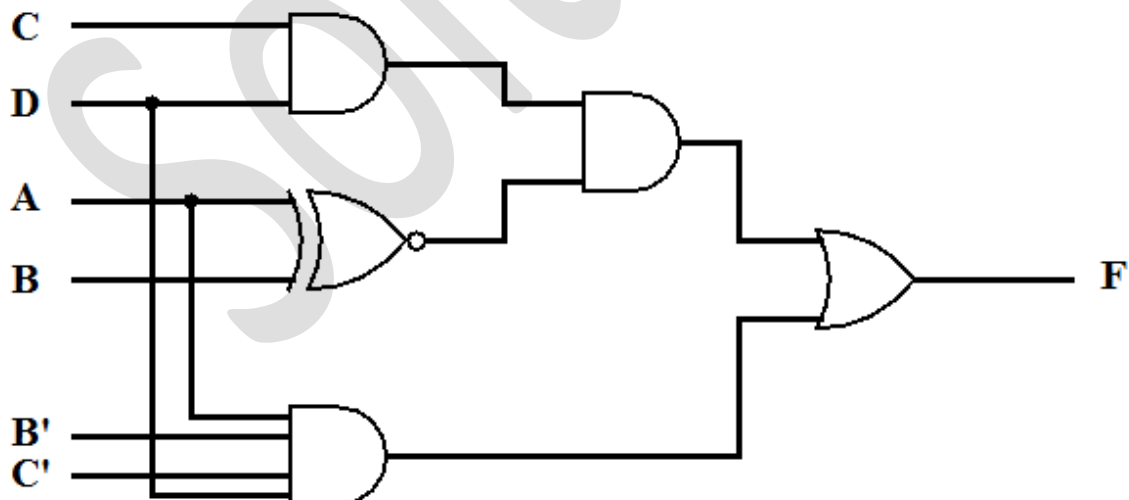



**Question Number 9****[2 + 5 + 2 + 1 = 10 Marks]**

Design a combinational circuit to count the number of 1's in the input sequence of 4 bits. For example, if the input is  $(1011)_2$  then the output should be 3  $(011)_2$ .

- No. of input(s) and output(s)
- Truth Table
- Simplified expression(s) of output(s)
- Logic Diagram

**4 Inputs and 3 output**

A	B	C	D	x	y	z
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	0	1	0
1	1	0	1	0	1	1
1	1	1	0	0	1	1
1	1	1	1	1	0	0

CD \ AB	00	01	11	10
00				
01				
11			1	
10				

$$x = ABCD$$

CD \ AB	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	


$$z = A \oplus B \oplus C \oplus D$$

CD \ AB	00	01	11	10
00			1	
01		1	1	1
11	1	1		1
10		1	1	1

$$y = ABC' + AB'D + ACD' + BC'D + BCD' + A'CD$$

$$y = A(BC' + B'D + CD') + B(C'D + CD') + A'CD$$
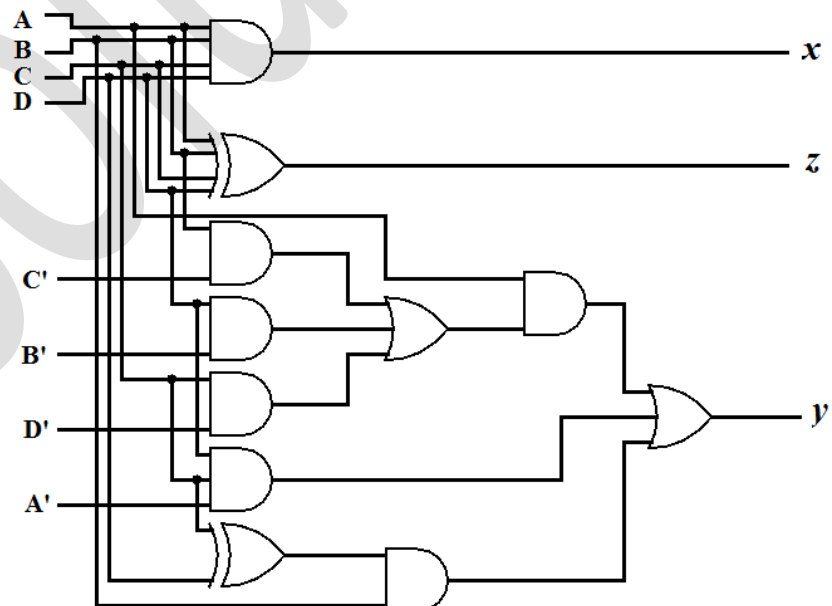
$$y = A(BC' + B'D + CD') + B(C \oplus D) + A'CD$$



**Question Number 10****[2 + 5 + 2 + 1 = 10 Marks]**

Design a combinational circuit to divide a 4-bit binary number ( $A_3A_2A_1A_0$ ) by a constant  $3_{10}$  and after the division produce the quotient as output. Complete your design by finding the:

- No. of input(s) and output(s)
- Truth Table
- Simplified expression(s) of output(s)
- Logic Diagram

**4 Inputs and 3 output**

$A_3$	$A_2$	$A_1$	$A_0$	$Q_2$	$Q_1$	$Q_0$
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	0	1
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	0	1	1
1	0	1	1	0	1	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	1

$A_3A_2$	$A_1A_0$	00	01	11	10
00					
01					
11		1	1	1	1
10					

$$Q_2 = A_3A_2$$

$A_3A_2$	$A_1A_0$	00	01	11	10
00					
01				1	1
11					
10		1	1	1	1

$$Q_2 = A_3A_2' + A_3'A_2A_1$$

$A_3A_2$	$A_1A_0$	00	01	11	10
00				1	
01		1	1		
11				1	
10		1	1	1	1

$$F = A_3'A_2A_1' + A_2'A_1A_0 + A_3A_2'A_0 + A_3A_2'A_1 + A_3A_1A_0$$

