



National University

of Computer and Emerging Sciences Chiniot -Faisalabad Campus



EE1005 – Digital Logic Design Quiz# 1

Instructor: Muhammad Adeel Tahir
Name: _____
Total Marks: 15 marks

Section: CS – 3N

Time: 20 Minutes

Roll Number:

2			-				
---	--	--	---	--	--	--	--

Instruction: Cuttings will lead to deductions in each part, use a rough sheet for your rough work.

Question 1: A circuit takes four inputs: *a, b, c, and d*. The three inputs *a, b, and c* represent the binary digits of the number (0-7), with *a* being the most significant bit. *d* is an odd-parity bit, meaning it ensures that the total number of 1s in *a, b, c, and d* is always **odd**. The circuit outputs 1 if the input **number is a prime** number, and 0 otherwise. A prime number is a number divisible only by itself and 1. 1 is considered prime, but 0 is not. Apply don't care carefully.
Implement the truth table for the above circuit [5 marks]
Implement the K-map for the truth table [3 marks]
Write the final simplified expression obtained from the k map. [2 marks]
Note: No cutting is allowed, it will be marked as wrong in case of cutting.

a	b	c	d	Output
0	0	0	0	x
0	0	0	1	0
0	0	1	0	1
0	0	1	1	x
0	1	0	0	1
0	1	0	1	x
0	1	1	0	x
0	1	1	1	1
1	0	0	0	0
1	0	0	1	x
1	0	1	0	x
1	0	1	1	1
1	1	0	0	x
1	1	0	1	0
1	1	1	0	1
1	1	1	1	x

		<i>c,d</i>			
		00	01	11	10
<i>a,b</i>	00	-	0	-	1
	01	1	-	1	-
	11	-	0	-	1
	10	0	-	1	-

$$f(a, b, c, d) = a'd' + c$$

For Rough Work Only (will not be checked)

Outputs:

1: The combination has an odd number of 1s and the 3-bit number (a, b, c) is prime.

0: The combination has an odd number of 1s but the 3-bit number (a, b, c) is not prime.

X(Don't care): The combination does not have an odd number of 1s (don't care condition).

Total Combinations: 16

Outputs is 1: Combinations where there is an odd number of 1s and the 3-bit number (a, b, c) is prime.

Outputs is 0: Combinations with an odd number of 1s but the 3-bit number (a, b, c) is not prime.

Outputs is Don't Care : All other combinations (even number of 1s).

Prime Number Check: The number represented by (a, b, c) (interpreted as a 3-bit binary number) must be one of [1, 2, 3, 5, 7], where 1 is considered prime and 0 is not prime.

Question 2:**[5 marks]**

Given the following Function F, perform the following parts carefully.


$$F(A, B, C, D) = \Sigma(0, 1, 2, 3, 6, 10, 11, 14)$$

Note: No cutting is allowed, it will be marked as wrong in case of cutting.

- a) Write down the min terms for function G that is the complement of the above function F:

$$G(A, B, C, D) = 4, 5, 7, 8, 9, 12, 13, 15$$

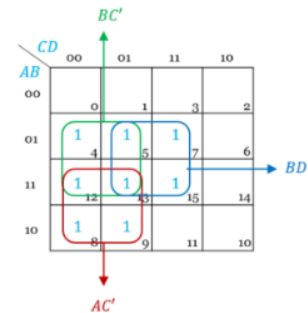- b) Plot G on K-map, write the final equation obtained from it: $AC' + BC' + BD$



Rough Work Only: