

EE1005 – Digital Logic Design

Quiz# 3

SOLUTION MANUAL

Q: An **M-bit** thermometer code for the number **k** consists of **(k) 1's** in the least significant bit positions and **(M – k) 0's** in more significant bit positions. A binary-to-thermometer code converter has **N inputs** and $2^N - 1$ **outputs**. It produces a $2^N - 1$ bit thermometer code for the number specified by the input. Design a combinational circuit for binary-to-thermometer code converter provided the number of inputs = 3 by finding the following:

Marking Criteria:

Inputs/Outputs : 1 mark

Truth Table: 5 marks

Equations: 4 marks

Circuit Diagram: 5 marks

Note: Incase truth table is wrong, question will receive 0 marks. (Binary Checking)

Those who tried to attempt it a little and got 1-2 values wrong , they may receive partial marks for the truth table.

No of Inputs: 3

No of Outputs: $2^3 - 1 = 7$

(1 marks)

Truth Table:

(5 marks)

From the definition above, we can fill the truth table. 0 will have zero 1s, 1 will have one 1s starting from the least significant bit, 2 will have two 1s and so on and so on.

| Decimal Digit | Inputs | | | Outputs | | | | | | |
|---------------|--------|----|----|---------|----|----|----|----|----|----|
| | B2 | B1 | B0 | T6 | T5 | T4 | T3 | T2 | T1 | T0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 2 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| 3 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 5 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 6 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 7 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

Equations:

(1.75 each = 4 marks)

Using k-maps to obtain the following equations, one is done rest was similar too.

| | | | | | |
|----|---|-------|----|----|----|
| | | B1 B0 | | | |
| | | 00 | 01 | 11 | 10 |
| B2 | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 1 | 1 | 1 |

B0

From k map: $T4 = B2.B0 + B2.B1$ Similarly,

$$T_6 = B_2.B_1.B_0$$

$$T_5 = B_2.B_1$$

$$T_3 = B_2$$

$$T_2 = B_2 + B_1.B_0$$

$$T_1 = B_2 + B_1$$

$$T_0 = B_2 + B_1 + B_0$$

$$T_5 = 1, \text{ iff } B_2 = 1, B_1 = 1$$

T_3 only depends on B_2

Circuit Diagram:

(5 marks)

