



## EE1005 – Digital Logic Design

### Quiz# 4

### SOLUTION MANUAL

**Total Marks: 20**

**Q:** In a simple copy machine, a stop signal, S, is to be generated to stop the machine operation and energize an indicator light whenever either of the following conditions exists: (1) there is no paper in the paper feeder tray; or (2) the two microswitches in the paper path are activated, indicating a jam in the paper path. The presence of paper in the feeder tray is indicated by a HIGH at logic signal P. Each of the microswitches produces a logic signal (Q and R) that goes HIGH whenever paper is passing over the switch to activate it. Design the logic circuit to produce a HIGH at output signal S for the stated conditions, and implement it using two input NAND gates only. **(10 marks)**

**Marking Criteria:** Note: Incase Truth table is wrong, the question will be marked as 0.

Correct Truth Table = 5 marks

Correct k-map = 3 marks

Correct Circuit = 2 marks

**Solution:**


The truth table is shown below, The S output will be a logic 1 whenever  $P = 0$  because this indicates no paper in the feeder tray. S will also be a 1 for the two cases where Q and R are both 1, indicating a paper jam. As the table shows, there are five different input conditions that produce a HIGH output

P	Q	R	S	
0	0	0	1	$\overline{P}\overline{Q}\overline{R}$
0	0	1	1	$\overline{P}\overline{Q}R$
0	1	0	1	$\overline{P}Q\overline{R}$
0	1	1	1	$\overline{P}QR$
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	1	$PQR$

		Q,R			
		00	01	11	10
P	0	1	1	1	1
	1	0	0	1	0

$$S = P' + QR$$

### Circuit Diagram:

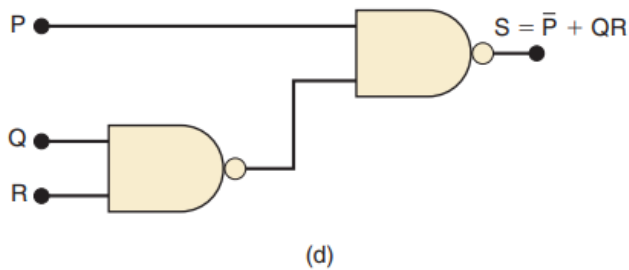

**Q2:** An analog-to-digital converter is monitoring the DC voltage ( $V_B$ ) of a 12-V storage battery on an orbiting spaceship. The converter's output is a four-bit binary number, ABCD, corresponding to the battery voltage in steps of 1 V, with A as the MSB. The converter's binary outputs are fed to a logic circuit that is to produce a HIGH output if the binary value is greater than 6; that is, the battery voltage is greater than 6 V. Design this logic circuit. **(10 marks)**

**Marking Criteria:** Note: Incase Truth table is wrong, the question will be marked as 0.

Correct Truth Table = 5 marks

Correct k-map = 3 marks

Correct Circuit = 2 marks

### Solution:

For each case in the truth table, we have indicated the decimal equivalent of the binary number represented by the ABCD combination. The output  $z$  is set equal to 1 for all those cases where the binary number is greater than 0110 (6). For all other cases,  $z$  is set equal to 0. Using k-map we can obtain the equation as followed:

	A	B	C	D	z
(0)	0	0	0	0	0
(1)	0	0	0	1	0
(2)	0	0	1	0	0
(3)	0	0	1	1	0
(4)	0	1	0	0	0
(5)	0	1	0	1	0
(6)	0	1	1	0	0
(7)	0	1	1	1	1 $\rightarrow \bar{A}BCD$
(8)	1	0	0	0	1 $\rightarrow A\bar{B}\bar{C}\bar{D}$
(9)	1	0	0	1	1 $\rightarrow A\bar{B}\bar{C}D$
(10)	1	0	1	0	1 $\rightarrow A\bar{B}C\bar{D}$
(11)	1	0	1	1	1 $\rightarrow A\bar{B}CD$
(12)	1	1	0	0	1 $\rightarrow AB\bar{C}\bar{D}$
(13)	1	1	0	1	1 $\rightarrow AB\bar{C}D$
(14)	1	1	1	0	1 $\rightarrow ABC\bar{D}$
(15)	1	1	1	1	1 $\rightarrow ABCD$



$$Z(A,B,C,D) = BCD + A$$

### Circuit Diagram:

